

# Management and analysis of physics datasets, Part. 1

## Fourth Laboratory

---

Antonio Bergnoli [bergnoli@pd.infn.it](mailto:bergnoli@pd.infn.it)

22/11/2021

## Laboratory Introduction

---

- Recap of the previous lectures
- Synchronous logic design
- inference in VHDL and State machines

1. **type** definition
2. other uses of **wait**
3. **if then else**

### Web resources

1. [https : //www.edaplayground.com/](https://www.edaplayground.com/)
2. [https : //vhdlwhiz.com/](https://vhdlwhiz.com/)
3. [https : //surf-vhdl.com/](https://surf-vhdl.com/)

### Free Books and Handbooks

4. VHDL Handbook **old but still good!!**
5. Free Range VHDL

## Synchronous Logic design

---

Neglecting temporary the *multi clock* systems, we assume the following statements as true:

1. there is a single clock in the system
2. we consider only one *sensitive edge* (rising or falling)
3. all the activity of the signals in the circuit occurs during the rising edge of the clock

In other words: only during a rising edge of the clock the *state* the system could change

# The RTL design

RTL stands for Register Trasfer Level

 


Figure 1: rtl example 1


 


Figure 3: rtl example 3

 



# Synchronizing the input

 


Figure 4: double flop

 


Figure 5: double flop wave

Why two flip flop and not one? (see next lectures, *metastability*)

### **Model the input synchronizer and test it**

1. write a VHDL source code for the synchronizer
2. write a testbench to validate the input synchronizer

## Inference in VHDL

---

### Inference informal definition

Inference is the process of transforming a high level description into a lower level representation (e.g: *rtl* level or *gate* level)

### From “Free Range VHDL”

(...) Modeling digital circuits with VHDL is a form of modern digital design distinct from schematic-based approaches. The programmer writes a loose description of what the final logic circuit should do and a language compiler, in this case called a synthesizer, attempts to **infer** what the actual final physical logic circuit should be. Novice programmers are not always able to convince the synthesizer to implement something that seems very clear in their minds. (...)

 


Figure 6: toggle state machine

 


Figure 7: toggle flip flop

# State machines source code (taken from “Free Range VHDL” book)

## Toggle flip flop as state machine

```
library IEEE;
use IEEE.std_logic_1164.all;           -- entity
entity my_fsm1 is
    port (TOG_EN, CLK, CLR : in  std_logic;
          Z1              : out std_logic);
end my_fsm1;
```

```
architecture fsm2 of my_fsm1 is
    type state_type is (ST0, ST1);
    signal state : state_type;
begin
    sync_proc : process(CLK)
    begin
        if (rising_edge(CLK)) then
            if (CLR = '1') then
                state <= ST0;
                Z1    <= '0';           -- pre-assign
            else
                case state is
                    when ST0 => -- items regarding state ST0
                        Z1 <= '0'; -- Moore output
                        if (TOG_EN = '1') then state <= ST1;
                        end if;
                    when ST1 => -- items regarding state ST1
                        Z1 <= '1'; -- Moore output
                        if (TOG_EN = '1') then state <= ST0;
                        end if;
                    when others => -- the catch-all condition
                        Z1    <= '0'; -- arbitrary; it should never
                        state <= ST0; -- make it to these two statements
                end case;
            end if;
        end if;
    end process sync_proc;
end fsm1;
```

## Homework

---

- build another state machine and try to model it in VHDL;
- build a testbench for it.